

30.5

$$(a) M = \frac{N_2 \Phi_{B_2}}{i_1} = \frac{(400)(0.0320 \text{ Wb})}{6.52 \text{ A}} = 1.96 \text{ H}$$

$$(b) \text{ When } i_2 = 2.54 \text{ A, } \Phi_{B_1} = \frac{i_2 M}{N_1} = \frac{(2.54 \text{ A})(1.96 \text{ H})}{700} \\ = 7.11 \times 10^{-3} \text{ Wb}$$

30.11

$$(a) |\mathcal{E}| = L \left( \frac{di_1}{dt} \right) = (0.260 \text{ H})(0.0180 \text{ A/s}) \\ = 4.68 \times 10^{-3} \text{ V}$$

(b) "a" is at a higher potential since the coil pushes current from b to a, and if replaced by a battery it would have the + terminal at "a".

30.22

$$(a) u = \frac{U}{\text{Vol}} = \frac{B^2}{2\mu_0} \Rightarrow \text{Volume} = \frac{2\mu_0 U}{B^2} \\ = \frac{2\mu_0 (3.60 \times 10^6 \text{ J})}{(0.600 \text{ T})^2} = 25.1 \text{ m}^3$$

$$(b) B^2 = \frac{2\mu_0 U}{\text{Vol}} = \frac{2\mu_0 (3.60 \times 10^6 \text{ J})}{(0.400 \text{ m}^3)} = 141.4 \text{ T}^2 \\ \Rightarrow B = 11.9 \text{ T}$$

30.28

(a) At  $t=0$ ,  $\mathcal{V}_{ab} = 0$  and  $\mathcal{V}_{bc} = 60 \text{ V}$

(b) As  $t \rightarrow \infty$ ,  $\mathcal{V}_{ab} \rightarrow 60 \text{ V}$  and  $\mathcal{V}_{bc} \rightarrow 0$

(c) When  $i = 0.150 \text{ A}$ ,  $\mathcal{V}_{ab} = iR = 36.0 \text{ V}$   
and  $\mathcal{V}_{bc} = 60.0 \text{ V} - 36.0 \text{ V} = 24.0 \text{ V}$

30.35

$$\begin{aligned}
 (a) \quad T &= \frac{2\pi}{\omega} = 2\pi\sqrt{LC} \\
 &= 2\pi\sqrt{(1.50\text{ H})(6.00 \times 10^{-5}\text{ F})} \\
 &= 0.0596\text{ s}
 \end{aligned}$$

$$\omega = 105\text{ rad/s}$$

$$\begin{aligned}
 (b) \quad Q &= CV = (6.00 \times 10^{-5}\text{ F})(12.0\text{ V}) \\
 &= 7.20 \times 10^{-4}\text{ C}
 \end{aligned}$$

$$\begin{aligned}
 (c) \quad U_0 &= \frac{1}{2}CV^2 = \frac{1}{2}(6.00 \times 10^{-5}\text{ F})(12.0\text{ V})^2 \\
 &= 4.32 \times 10^{-3}\text{ J}
 \end{aligned}$$

$$(d) \quad \text{At } t=0, q = Q = Q \cos(\omega t + \phi) \Rightarrow \phi = 0$$

$$\begin{aligned}
 t = 0.0230\text{ s}, \quad q &= Q \cos(\omega t) \\
 &= (7.20 \times 10^{-4}\text{ C}) \cos\left(\frac{0.0230\text{ s}}{\sqrt{(1.50\text{ H})(6.00 \times 10^{-5}\text{ F})}}\right) \\
 &= -5.43 \times 10^{-4}\text{ C}
 \end{aligned}$$

Signs on plates are opposite to those at  $t=0$ .

$$(e) \quad t = 0.0230\text{ s}, \quad i = \frac{dq}{dt} = -\omega Q \sin \omega t$$

$$i = - \frac{7.20 \times 10^{-4}\text{ C}}{\sqrt{(1.50\text{ H})(6.00 \times 10^{-5}\text{ F})}} \sin\left(\frac{0.0230\text{ s}}{\sqrt{(1.50\text{ H})(6.00 \times 10^{-5}\text{ F})}}\right)$$

$$= -0.0499\text{ A}$$

Positive charge flowing away from the plate that had positive charge at  $t=0$ .


$$(f) \quad \text{Capacitor: } U_C = \frac{q^2}{2C} = \frac{(5.43 \times 10^{-4}\text{ C})^2}{2(6.00 \times 10^{-5}\text{ F})} = 246 \times 10^{-3}\text{ J}$$

$$\begin{aligned}
 \text{Inductor: } U_L &= \frac{1}{2}Li^2 = \frac{1}{2}(1.50\text{ H})(0.0499\text{ A})^2 \\
 &= 1.87 \times 10^{-3}\text{ J}
 \end{aligned}$$

30.65

(a) Initially, the capacitor behaves like a short circuit and the inductor like an open circuit.

The simplified circuit becomes

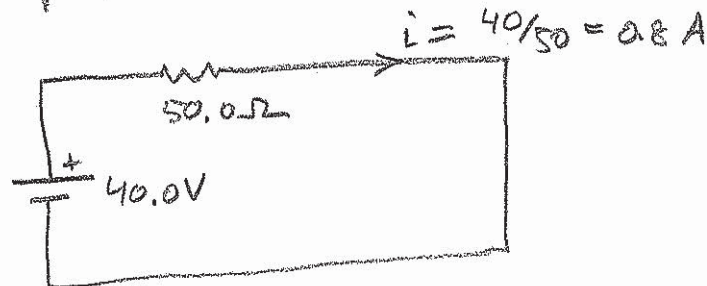

$$\text{So } V_1 = 40.0 \text{ V}$$

$$V_2 = 0$$

$$V_3 = 0$$

$$A_2 = 0$$

$$A_1 = 0.8 \text{ A}$$

$$A_3 = 0$$


$$V_5 = 0$$

$$A_4 = A_1 = 0.8 \text{ A}$$

$$V_4 = 0$$

(b) Long after  $S$  is closed, the capacitor stops the current through  $A_4$  and  $\frac{di}{dt} \rightarrow 0$ .

So the simplified circuit becomes

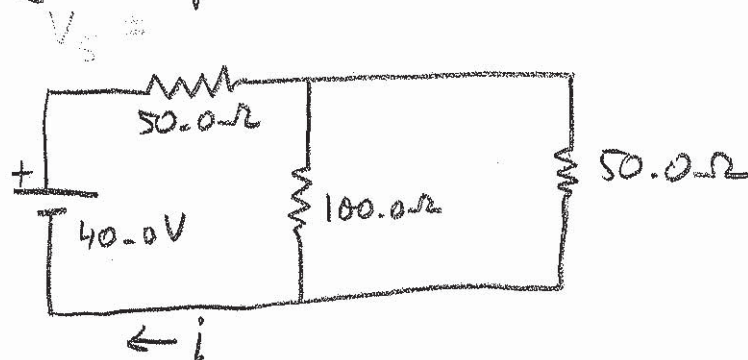

And therefore  $i = \frac{V}{R}$  where

$$R = 50.0 \Omega + \frac{1}{\frac{1}{100.0 \Omega} + \frac{1}{50.0 \Omega}}$$

$$= 83.3 \Omega$$

so  $i = \frac{40.0 \text{ V}}{83.3 \Omega} = 0.48 \text{ A}$ .

Thus,  $V_1 = (50.0 \Omega)(0.48 \text{ A}) = 24.00 \text{ V}$

$$V_2 = 0$$

$$A_1 = 0.48 \text{ A}$$

$$V_5 = V - V_1 = 16.0 \text{ V}$$

$$A_4 = 0$$

$$A_2 = \frac{1}{3} A_1 = 0.16 \text{ A}$$

$$A_3 = \frac{2}{3} A_1 = 0.32 \text{ A}$$

$$V_3 = (100 \Omega)(0.16 \text{ A}) = 16 \text{ V}$$

$$V_4 = (500 \Omega)(0.32 \text{ A}) = 16 \text{ V}$$