

31.7

$$V_c = \frac{I}{\omega C} \Rightarrow C = \frac{I}{\omega V_c} = \frac{(0.850 \text{ A})}{2\pi(60 \text{ Hz})(170 \text{ V})}$$

$$= 1.32 \times 10^{-5} \text{ F.}$$

31.15

$$(a) Z = \sqrt{R^2 + (\omega L - 1/\omega C)^2}$$

$$Z = \sqrt{(200 \Omega)^2 + \left[(250 \text{ rad/s})(0.0400 \text{ H}) - \frac{1}{(250 \text{ rad/s})(6.00 \times 10^{-6} \text{ F})} \right]^2}$$

$$= 601 \Omega.$$

$$(b) I = \frac{V}{Z} = \frac{30 \text{ V}}{601 \Omega} = 0.0499 \text{ A}$$

$$(c) \phi = \arctan \left[\frac{\omega L - 1/\omega C}{R} \right]$$

$$= \arctan \left[\frac{100 \Omega - 667 \Omega}{200 \Omega} \right]$$

$$= -70.6^\circ$$

and the voltage lags the current.

$$(d) V_R = IR = (0.0499 \text{ A})(200 \Omega) = 9.98 \text{ V}$$

$$V_L = I\omega L = (0.0499 \text{ A})(250 \text{ rad/s})(0.400 \text{ H})$$

$$= 4.99 \text{ V}$$

$$V_C = \frac{I}{\omega C} = \frac{(0.0499 \text{ A})}{(250 \text{ rad/s})(6.00 \times 10^{-6} \text{ F})}$$

$$= 33.3 \text{ V}$$

(e) Since C is storing charges, its voltage lags the source voltage. Its voltage will peak after the source voltage.

31.24

$$\begin{aligned}
 P_{\text{av}} &= \frac{V_{\text{rms}}^2}{Z} \cos \phi \\
 &= \frac{V_{\text{rms}}^2}{Z} \frac{R}{Z} \\
 &= \frac{V_{\text{rms}}^2}{Z^2} R = \frac{(80.0 \text{ V})^2}{(105 \Omega)^2} (75.0 \Omega) \\
 &= 43.5 \text{ W}
 \end{aligned}$$

31.35

$$(a) \quad \frac{N_1}{N_2} = \frac{120}{12} = 10.$$

$$(b) \quad I_{\text{rms}} = \frac{V_{\text{rms}}}{R} = \frac{12.0 \text{ V}}{5.00 \Omega} = 2.40 \text{ A}$$

$$(c) \quad P_{\text{av}} = I_{\text{rms}} V_{\text{rms}} = (2.40 \text{ A})(12.0 \text{ V}) = 28.8 \text{ W}$$

$$(d) \quad R = \frac{V_{\text{rms}}^2}{P} = \frac{(120 \text{ V})^2}{28.8 \text{ W}} = 500 \Omega,$$

which is the same as

$$(5.00 \Omega) \left(\frac{N_1}{N_2} \right)^2 = (5.00 \Omega) \left(\frac{120}{12.0} \right)^2 = 500 \Omega.$$

31.39

$$\begin{aligned}
 \phi &= \arctan \left(\frac{\omega L}{R} \right) \\
 \Rightarrow L &= \frac{R}{\omega} \tan \phi = \frac{R}{2\pi f} \tan \phi \\
 &= \frac{(48.0 \Omega)}{2\pi (80 \text{ Hz})} \tan (52.3^\circ) \\
 &= 0.124 \text{ H}
 \end{aligned}$$

31.52

$$V_{out} = V_c = \frac{I}{\omega C}$$

$$\Rightarrow \frac{V_{out}}{V_s} = \frac{I}{\omega C \sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

If ω is large, $\frac{V_{out}}{V_s} \approx \frac{1}{\omega C \sqrt{(\omega L)^2}} = \frac{1}{(LC) \omega^2}$

If ω is small, $\frac{V_{out}}{V_s} \approx \frac{1}{\omega C \sqrt{(1/\omega C)^2}} = \frac{\omega C}{\omega C} = 1$