

24.1

$$(a) \quad E = \frac{\Delta V}{d}$$

$$\Delta V = E \cdot d = (4.00 \times 10^6 \text{ V/m}) (2.5 \times 10^{-3} \text{ m}) \\ = 10^4 \text{ V}$$

$$(b) \quad E = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

$$A = \frac{Q}{\epsilon_0 E} = \frac{8.0 \times 10^{-10} \text{ C}}{(8.85 \times 10^{-12} \text{ C}^2/\text{N}\cdot\text{m}^2)(4.00 \times 10^6 \text{ V/m})} \\ = 2.260 \times 10^{-5} \text{ m}^2$$

$$(c) \quad C = \frac{Q}{V} = \frac{8.0 \times 10^{-10} \text{ C}}{10^4 \text{ V}}$$

$$= 8.0 \times 10^{-14} \text{ C/V} = 80 \text{ pF.}$$

24.14

(a) for 2 concentric shells, the capacitance is

$$C = \frac{1}{k} \left(\frac{r_a r_b}{r_b - r_a} \right)$$

$$k C r_b - k C r_a = r_a r_b$$

$$r_b = \frac{k C r_a}{k C - r_a}$$

$$= \frac{k (116 \times 10^{-12} \text{ F})(0.150 \text{ m})}{k (116 \times 10^{-12} \text{ F}) - 0.150 \text{ m}}$$

$$= 0.175 \text{ m}$$

$$(b) \quad V = 220 \text{ V, and } Q = CV = (116 \times 10^{-12} \text{ F})(220 \text{ V}) \\ = 2.55 \times 10^{-8} \text{ C}$$

24.20

(a) C_1 & C_2 are in parallel, so have same potential.

$$V = \frac{Q_2}{C_2} = \frac{40.0 \times 10^{-6} \text{ C}}{3.00 \times 10^{-6} \text{ F}} = 13.33 \text{ V}$$

$$\therefore Q_1 = VC_1 = (13.33 \text{ V})(6.00 \times 10^{-6} \text{ F}) = 80.0 \times 10^{-6} \text{ C}$$

C_3 is in series with parallel combination of C_1 & C_2 .

So Q_3 must equal their combined charge:

$$\begin{aligned} Q_3 &= 40.0 \times 10^{-6} \text{ C} + 80.0 \times 10^{-6} \text{ C} \\ &= 120.0 \times 10^{-6} \text{ C} \end{aligned}$$

$$(b) \quad \frac{1}{C_{\text{tot}}} = \frac{1}{C_{\parallel}} + \frac{1}{C_3} = \frac{1}{9.00 \times 10^{-6} \text{ F}} + \frac{1}{5.00 \times 10^{-6} \text{ F}}$$

$$C_{\text{tot}} = 3.21 \mu\text{F}. \quad \text{Also, } V_{ab} = \frac{Q_{\text{tot}}}{C_{\text{tot}}} = \frac{120.0 \times 10^{-6} \text{ C}}{3.21 \times 10^{-6} \text{ F}} = 37.4 \text{ V}$$

24.29

Applied voltage = V .

Each capacitor has capacitance C .

$$U = \frac{1}{2} CV^2.$$

(a) Series:
$$U_s = 2 \left(\frac{1}{2} C \left[\frac{V}{2} \right]^2 \right)$$
$$= \frac{1}{4} CV^2$$

Parallel:
$$U_p = 2 \left(\frac{1}{2} CV^2 \right)$$
$$= CV^2$$

$$\therefore U_p = 4U_s$$

(b) $Q = CV$

$$\therefore Q_s = 2 (C \left[\frac{V}{2} \right]) = CV$$

$$Q_p = 2 (CV) = 2CV$$

$$\therefore Q_p = 2Q_s$$

(c) $E = V/d$

$$\therefore E_s = \frac{V}{2d}$$

$$E_p = \frac{V}{d}$$

$$\therefore E_p = 2E_s$$

24.57

$$(a) \quad \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2 + \left(\frac{1}{C_3} + \frac{1}{C_4}\right)^{-1}} + \frac{1}{C_5}$$

$$\therefore C_1 = C_5 = 2C_2 \text{ and} \\ C_2 = C_3 = C_4 \text{ so}$$

$$\frac{1}{C_{eq}} = \frac{2}{C_1} + \frac{2}{3C_2} = \frac{5}{3} C_2^{-1}$$

$$\therefore C_{eq} = \frac{3}{5} C_2 = 2.52 \mu\text{F}$$

$$(b) \quad Q = CV = (2.52 \mu\text{F})(220 \text{ V}) \\ = 5.54 \times 10^{-4} \text{ C} = Q_1 = Q_5$$

$$\therefore V_1 = V_5 = (5.54 \times 10^{-4} \text{ C}) / (8.4 \times 10^{-6} \text{ F}) = 66 \text{ V}$$

$$\text{So } V_2 = 220 - 2(66) = 88 \text{ V}$$

$$Q_2 = (88 \text{ V})(4.2 \mu\text{F}) = 3.70 \times 10^{-4} \text{ C}$$

$$\text{Also, } V_3 = V_4 = \frac{1}{2}(88 \text{ V}) = 44 \text{ V}$$

$$\therefore Q_3 = Q_4 = (44 \text{ V})(4.2 \mu\text{F}) = 1.85 \times 10^{-4} \text{ C.}$$